

Working of circuit

A	B	Q ₁	Q ₂	Y = Output
0	0	OFF	OFF	1
0	1	OFF	ON	0
1	0	ON	OFF	0
1	1	ON	ON	0

RTL Circuit consists of Resistor & transistor. The figure shows 2 Input RTL NOR gate. emitters of both transistor are connected to a common ground. & collectors of both transistor are tied through a common collector Resistor R_C to a supply Voltage V_{CC} . The Resistor R_C is commonly known as ^{Passive} pull up Resistor.

(711) Emitter coupled logic family (ECL)

The TTL family uses transistors operating in saturation mode. As a result, there is switching speed is limited by storage delay time associated with Transistor.

Sat → normal mode
mode
It takes time to stop in ECL to go into saturation mode


That is driven into the saturation.

Another logic family has been developed that prevents transistor saturation thereby increasing overall switching speed. This logic family is called Emitter coupled Transistor or current mode coupled logic family.

Characteristics of ECL:

- (1) It is the fastest logic family.
- (2) The propagation delay is less than 1 nanosecond.
- (3) Transistors are not allowed to go into saturation mode so that logical levels are kept close to each other.
- (4) A logical levels are kept close to each other, noise margin is reduced & it is difficult to achieve good noise immunity.
- (5) Another disadvantage of this approach is that power consumption is more.

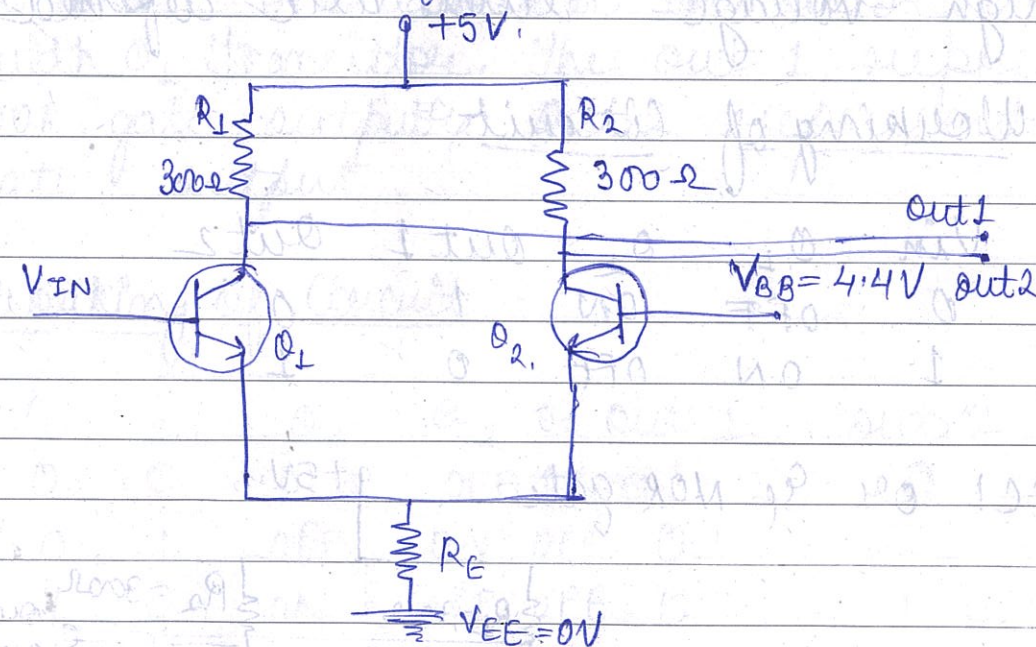(a) Basic ECL Circuit of Inverter/ Buffer Circuit



V_{IN} → Input of Circuit

Out 1 → Output of Inverter NOT gate

Out 2 → Output of Buffer Circuit

Voltage level required at Input side:

Logic 1 → 4.4V

Logic 0 → 3.6V